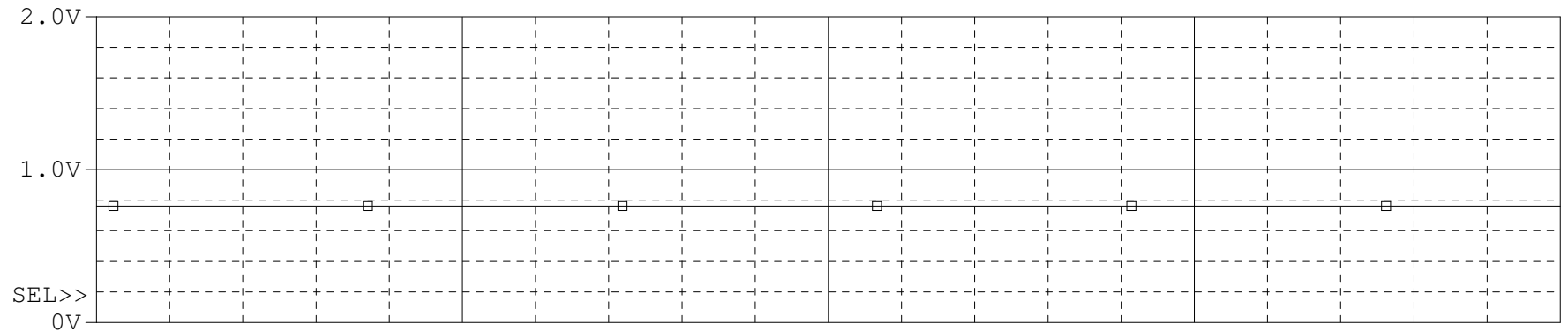


One Transistor Current Source


Date/Time run: 04/16/13 19:33:35

Temperature: 27.0


(A) one transistor.dat (active)



□ V(2)

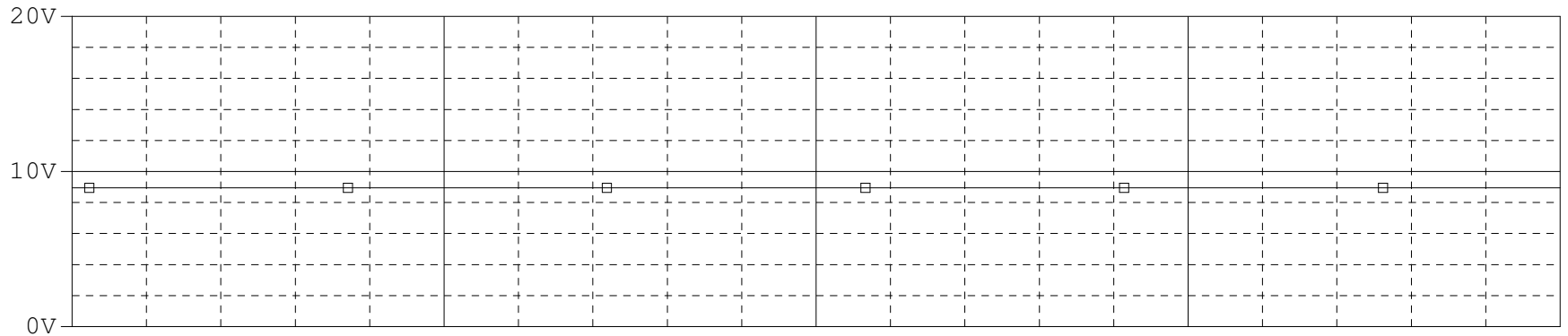

□ V(3)

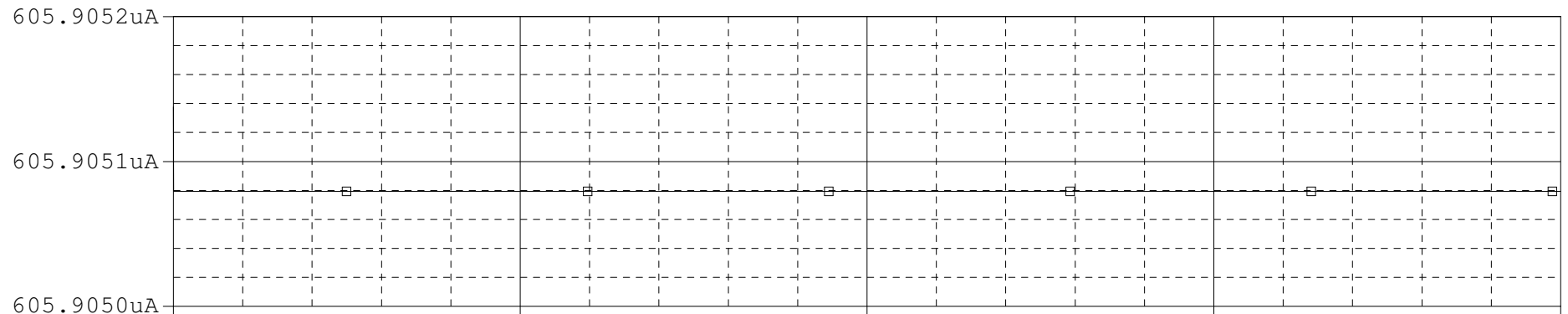

□ IC(Q1)

Time